

Google



**Next Semester के Latest Papers सबसे
पहले Download करने के लिए आप हमें
Contact भी कर सकते हैं**

Whatsapp No : 8076723805

Email : dm8076723805@gmail.com

Section C

4. (a) Explain the circuit configuration of C.E. transistor. Define its static and dynamic current amplification factors. Hence derive a relation between I_C , I_B and I_{CEO} . **8**
- (b) A transistor has $\alpha = 0.96$ and a collector leakage current I_{co} of $1 \mu A$. Calculate I_c and I_b , if $I_e = 1 \text{ mA}$. **8**
5. (a) What is D.C. load line ? How is it drawn ? What is the physical significance of this line ? **8**
- (b) Explain input and output characteristics of common collector configuration. **8**

Section D

6. (a) What is need of stabilisation in transistors ? Hence explain the working and analytical analysis of a transistor with voltage divider biasing. **8**

J-52553

4

Roll No.

Exam Code : J-21

Subject Code—52553

B. Sc. EXAMINATION

(Main/Reappear) (Batch 2018 Onwards)

(Third Semester)

PHYSICS

CPL-303

Course–VI

Semiconductor Devices

Time : 3 Hours

Maximum Marks : 80

Note : Attempt *Five* questions in all. Q. No. 1 is compulsory. All questions carry equal marks.

Section A

1. (a) Draw energy level diagram for P type semiconductor and comment. Why acceptor level is close to Valence Band ? **2**

(5-08-15-0721) J-52553

P.T.O.

- (b) Draw V-I characteristics of an Ideal Diode. 2
- (c) α Parameter (C. B. current gain) of a transistor is 0.97. Find the value of β for the same transistor. 2
- (d) What is Q-point in transistor characteristics ? What is the significance of Q-point ? 2
- (e) Differentiate between class A and class B amplifier on the basis of Q-point. 2
- (f) Name the devices used for the following operations : 2
- (i) High voltage A.C. to low voltage A.C. converter
- (ii) D.C. to A.C. converter.
- (g) Why is NPN transistor preferred over PNP transistor ? 2
- (h) Why two Diodes connected back to back cannot act as a transistor ? Write *two* parameters in support of your answer. 2

J-52553

2

Section B

2. (a) Explain the formation of Potential Barrier across an unbiased P-N Junction Diode. Also draw graph for Potential vs. distance along the depletion region for Si and Ge diodes. 8
- (b) What is Zener diode ? Differentiate between Zener and Avalanche Breakdown. Also explain the working of Zener Diode as a voltage stabiliser. 8
3. (a) Derive expressions for the following for a full wave central tap rectifier :
 (i) Average value of output current 4
 (ii) R.M.S. value of output current 4
 (iii) Ripple factor. 2
- (b) A load of $6\text{ k}\Omega$ is connected across the output of a full wave rectifier. Diodes are having forward resistance of $50\ \Omega$. If peak value of voltage supplied is 300V , find ripple factor. 6

(5-08-16-0721) J-52553

3

P.T.O.

- (c) In an inverting amplifier circuit $R_i = 2 \text{ k}\Omega$, $R_f = 6 \text{ k}\Omega$. If $V_i = 2\text{V}$, find output voltage and input current. 4
9. (a) Explain the working of an OP-Amp as
(i) Inverting Amplifier (ii) As Integrator. 12
- (b) In a non-inverting amplifier $R_i = 4 \text{ k}\Omega$, $R_f = 10 \text{ k}\Omega$. Find the value of voltage gain. 4

- (b) A certain amplifier has voltage gain of 10 dB. If the input signal voltage is 0.3V, what is output voltage ? (Given $\text{Antilog}(0.5) = 3.16$) ? 4
- (c) An amplifier has a voltage gain of 1000 without feedback. The gain reduces to 150 with negative feedback. Find feedback fraction (β) of the amplifier. 4
7. (a) Explain Barkhausen criteria for sustained oscillations. 4
- (b) The voltage gain of an amplifier is 100. If we apply a negative feedback with $\beta = 0.03$, find its new gain. 4
- (c) Explain the circuit and operation of Colpitts oscillator. 8

Section E

8. (a) Define CMRR for an OP-Amp. What is its physical significance ? 4
- (b) Explain open loop and closed loop gain in inverting mode OP-Amp. 8